

---

---

---

---

---



mechanical oscillators: Energy is converted between kinetic and potential.

Electrical oscillators: Energy is converted between electric ( $\vec{E}$  field) and magnetic ( $\vec{B}$  field).

① capacitor: device that stores energy in an electric field.

→ Ex: parallel plate capacitor.

Each small volume of space ( $dV$ ) with an electric field  $\vec{E}$  stores a small amount of electric energy ( $dU_E$ ):

$$dU_E = \frac{1}{2} \epsilon_0 |\vec{E}|^2 dV, \quad U_E = \frac{1}{2} \epsilon_0 \int |\vec{E}|^2 dV$$

↑  
Big  $U$   
↳ energy

↳  $U_E$   
↳ small  $U$  → energy density.

density of free space; unit:  $\frac{J}{m^3}$ .

The total energy stored is:

$$\text{"big } U" \rightarrow U_E = \int_{R^3} \frac{1}{2} \epsilon_0 |\vec{E}|^2 dV = \frac{1}{2} CV^2 = \frac{Q^2}{2C} = \frac{1}{2} QV.$$

② Inductor: A device that stores energy in magnetic field.

→ Ex: A simple solenoid.

$$\therefore dU_B = \frac{1}{2\mu_0} |\vec{B}|^2 dV \quad ; \quad u_B = \frac{1}{2\mu_0} |\vec{B}|^2.$$

$$\therefore U_B = \int_{R^3} \frac{1}{2\mu_0} |\vec{B}|^2 dV = \frac{1}{2} LI^2.$$

↳ self inductance.


Voltage rules:

capacitor:  $|V_C| = \left| \frac{1}{C} \cdot Q \right|$

Inductor:  $|V_L| = \left| -\frac{d\Phi_B}{dt} \right| = \left| -\frac{d(LI)}{dt} \right| = \left| L \frac{dI}{dt} \right|.$

LC oscillator:

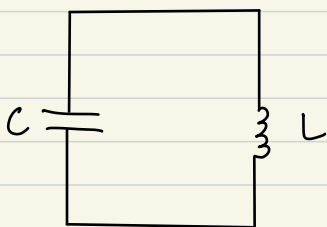→ Simplest electric oscillator. Energy exchanged between electric and magnetic.



from voltage loop rule:

$$V_C + V_L = 0$$

$$\Rightarrow \frac{q}{C} + L \frac{dq}{dt} = 0$$

$$\Rightarrow \frac{q}{C} + L \frac{d^2 q}{dt^2} = 0$$

$$\therefore \frac{1}{LC} q + \frac{d^2 q}{dt^2} = 0. \rightarrow \text{equation of the SHO.}$$

$$\therefore q(t) = q_0 e^{i(\omega_0 t + \delta)} ; \quad \omega_0 \equiv \frac{1}{\sqrt{LC}}.$$

→  $q_0$ ,  $\delta$  are determined by initial conditions.

$$\therefore I(t) = \dot{q}(t) = (i\omega_0) (q_0 e^{i(\omega_0 t + \delta)})$$

$$= i\omega_0 q(t).$$

↳ current has a phase shift of  $90^\circ$  compared to charge.

Energy:

$$U_E = \frac{1}{2C} q^2 = \frac{1}{2C} [q_0 \cos(\omega_0 t + \delta)]^2$$

$$= \frac{q_0^2}{2C} \cos^2(\omega_0 t + \delta).$$

$$U_B = \frac{1}{2} LI^2 = \frac{1}{2} L [\text{Re}(q_0 i \omega_0 e^{i(\omega_0 t + \delta)})]^2$$

$$= \frac{1}{2} L [-\omega_0 \sin(\omega_0 t + \delta) q_0]^2$$

$$= \frac{1}{2} q_0^2 \omega_0^2 L \sin^2(\omega_0 t + \delta)$$

$$= \frac{q_0^2}{2C} \sin^2(\omega_0 t + \delta).$$


$$\therefore \text{total energy: } U_E + U_B = \frac{q_0^2}{2C} [\cos^2(\omega_0 t + \delta) + \sin^2(\omega_0 t + \delta)]$$

$$= \frac{q_0^2}{2C}$$

Note:

mass with no friction  $\rightarrow$  LC circuit  
 $\downarrow$

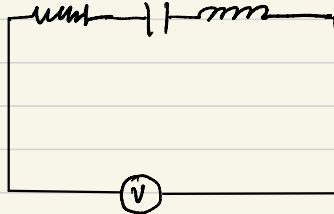with damping & driving  $\rightarrow$  LCR with power supply.



$$V = V_d \cos(\omega t)$$

$$\therefore iR + L \frac{di}{dt} + \frac{q}{C} = V_d \cos(\omega t)$$

$$\Rightarrow R \frac{dq}{dt} + L \frac{d^2q}{dt^2} + \frac{q}{C} = V_d \cos(\omega t)$$

$$\Rightarrow \ddot{q} + \frac{R}{L} \dot{q} + \frac{1}{LC} q = \frac{V_d}{L} \cos(\omega t)$$

$$\Rightarrow \ddot{q} + r\dot{q} + \omega^2 q = V \cos(\omega t)$$

$$\text{where } r = \frac{R}{L} ; \omega^2 = \frac{1}{LC} ; V = \frac{V_d}{L}$$

$$q(t) = \underset{\substack{\uparrow \\ \text{transient}}}{q_h(t)} + \underset{\substack{\uparrow \\ \text{steady state}}}{q_p(t)}$$

$$\therefore q(t) = Q_h e^{-\frac{r}{2}t} \cos(\omega_h t + \theta) + Q_p \cos(\omega t + \phi)$$

$\hookrightarrow \sqrt{\omega^2 - \frac{r^2}{4}}$

$$\therefore Q_p = \frac{V}{\sqrt{(\omega_0^2 - \omega_p^2)^2 - R^2 \omega_p^2}}$$

$$\tan(\phi) = \frac{-R\omega_p}{\omega_0^2 - \omega_p^2}$$

$$\begin{aligned} \langle P_{\text{driving}} \rangle &= \frac{1}{2} b (\omega_p Q_p)^2 = \frac{1}{2} R (\omega_p Q_p)^2 \\ &= \frac{1}{2} R \omega_p^2 \frac{V^2}{(\omega_0^2 - \omega_p^2)^2 + \frac{R^2}{L^2} \omega_p^2} \end{aligned}$$